

Corrigé de l'examen final BE 522

Exercice 1 4 PS

* $v(t) = V_m \sin \omega t$ 1

$$\bar{V} = \frac{2}{T} \int_0^{\frac{T}{2}} V_m \sin \omega t dt = \frac{2V_m}{T} \left[\frac{1}{\omega} (-\cos \omega t) \right]_0^{\frac{T}{2}}$$

$$= \frac{2V_m}{T} \cdot \frac{T}{2\omega} (-\cos \omega \cdot \frac{T}{2} + 1) = \frac{2V_m}{T} \cdot \frac{T}{2\pi} \cdot 2$$

$$\Rightarrow \boxed{\bar{V} = \frac{2V_m}{\pi}}$$
 1


* $V^2 = \frac{2}{T} \int_0^{\frac{T}{2}} V_m^2 \sin^2 \omega t dt = \frac{2V_m^2}{T} \int_0^{\frac{T}{2}} \left(\frac{1}{2} - \cos \frac{2\omega t}{2} \right) dt$

$$= \frac{2V_m^2}{T} \left[\frac{t}{2} - \frac{\sin 2\omega t}{4\omega} \right]_0^{\frac{T}{2}} = \frac{2V_m^2}{T} \left[\frac{T}{4} - \frac{\sin 2\omega}{4\omega} \right]_0^{\frac{T}{2}}$$

Car $\sin 2\pi - \sin 0 = 0 = 1 - 1$

$$\Rightarrow V^2 = \frac{2V_m^2}{T} \cdot \frac{T}{4} \Rightarrow \boxed{V = \frac{V_m}{\sqrt{2}}}$$
 2

Exercice 2 6 PS

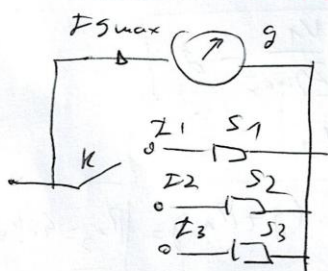

1) Par définition $K_i = \frac{I_{cal}}{I_{gmax}}$ 1

$$K_1 = \frac{I_1}{I_{gmax}} \Rightarrow K_1 = \frac{0,5}{0,5 \cdot 10^{-3}} \Rightarrow \boxed{K_1 = 1000}$$

$$K_2 = \frac{I_2}{I_{gmax}} = \frac{0,2}{0,5 \cdot 10^{-3}} \Rightarrow \boxed{K_2 = 400}$$

$$K_3 = \frac{I_3}{I_{gmax}} = \frac{0,05}{0,5 \cdot 10^{-3}} \Rightarrow \boxed{K_3 = 100}$$

2

$$2/x \quad g I_{gmax} = S_1 (I_1 - I_{gmax}) \Rightarrow \boxed{S_1 = \frac{g I_{gmax}}{I_1 - I_{gmax}}} \quad (1)$$

$$\Rightarrow S_1 = \frac{50 \cdot 0,5 \cdot 10^{-3}}{0,5 - 0,5 \cdot 10^{-3}} \Rightarrow \boxed{S_1 = 0,05 \Omega}$$

de même pour S_2 et S_3


$$g \cdot I_{gmax} = S_2 (I_2 - I_{gmax}) \Rightarrow \boxed{S_2 = \frac{g I_{gmax}}{I_2 - I_{gmax}}} \quad (1)$$

$$S_2 = \frac{50 \cdot 0,5 \cdot 10^{-3}}{0,2 - 0,5 \cdot 10^{-3}} \Rightarrow \boxed{S_2 = 0,13 \Omega}$$

$$g I_{gmax} = S_3 (I_3 - I_{gmax}) \Rightarrow \boxed{S_3 = \frac{g I_{gmax}}{I_3 - I_{gmax}}} \quad (2)$$

$$S_3 = \frac{50 \cdot 0,5 \cdot 10^{-3}}{0,05 - 0,5 \cdot 10^{-3}} \Rightarrow \boxed{S_3 = 0,5 \Omega}$$

Exercice 3 8pts

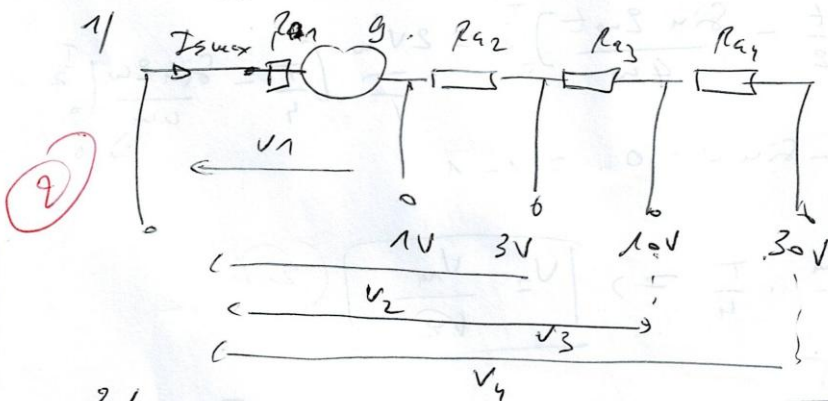

3/ Résistance spécifique

$$r_2 = \frac{R_k2}{V_1} = \frac{g + R_{k1}}{1}$$

$$\boxed{r_2 = 20000 \Omega/V}$$

$$2/x \quad V_1 = g I_{gmax} + R_{k1} I_{gmax} \Rightarrow \boxed{R_{k1} = \frac{V_1}{I_{gmax}} - g}$$

$$\Rightarrow R_{k1} = \frac{1}{50 \cdot 10^{-6}} - 10000 \Rightarrow \boxed{R_{k1} = 19 k\Omega} \quad (1)$$

$$2 \quad V_2 = (g + R_{k1} + R_{k2}) I_{gmax} \Rightarrow \boxed{R_{k2} = \frac{V_2}{I_{gmax}} - (g + R_{k1})} \Rightarrow \boxed{R_{k2} = 40 k\Omega} \quad (1)$$

$$3 \quad V_3 = (g + R_{k1} + R_{k2} + R_{k3}) I_{gmax} \Rightarrow \boxed{R_{k3} = \frac{V_3}{I_{gmax}} - (g + R_{k1} + R_{k2})} \Rightarrow \boxed{R_{k3} = 140 k\Omega} \quad (2)$$

$$4 \quad V_4 = (g + R_{k1} + R_{k2} + R_{k3} + R_{k4}) I_{gmax} \Rightarrow \boxed{R_{k4} = \frac{V_4}{I_{gmax}} - (g + R_{k1} + R_{k2} + R_{k3})} \Rightarrow \boxed{R_{k4} = 400 k\Omega} \quad (2)$$